

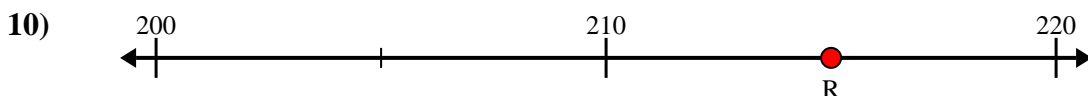
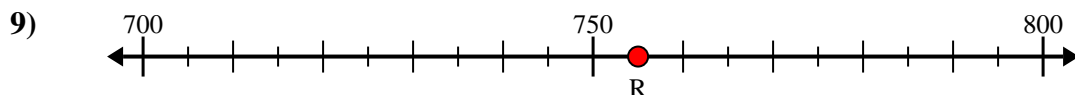
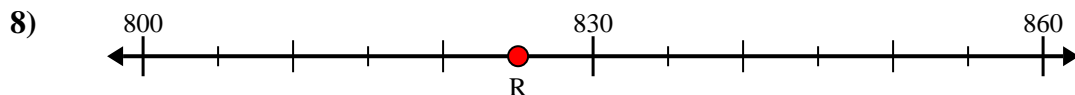
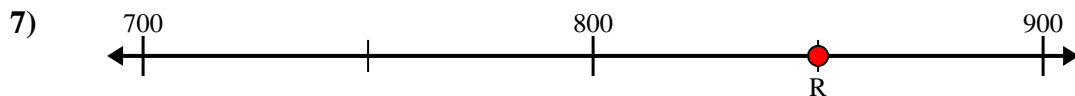
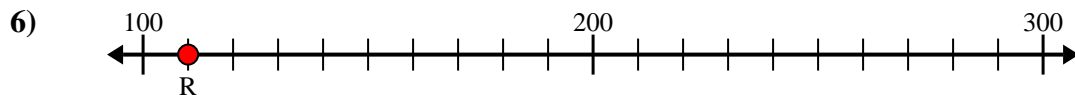
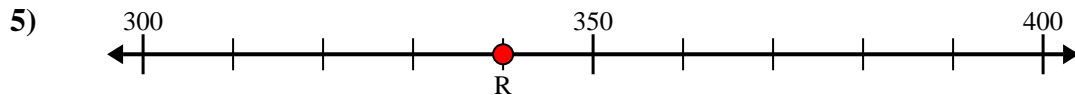
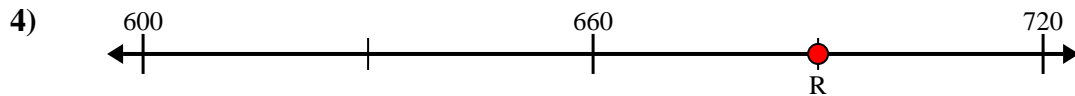
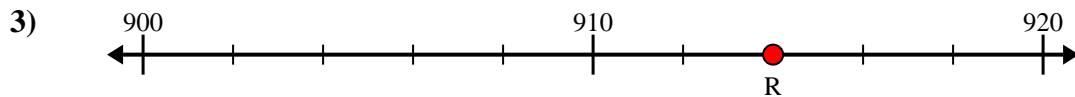


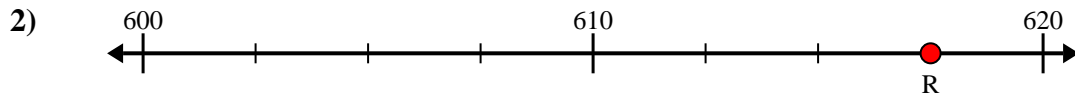

Find the value of R.

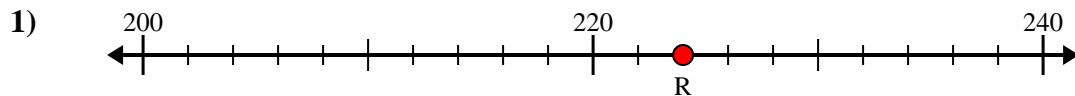


Answers

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Find the value of R.

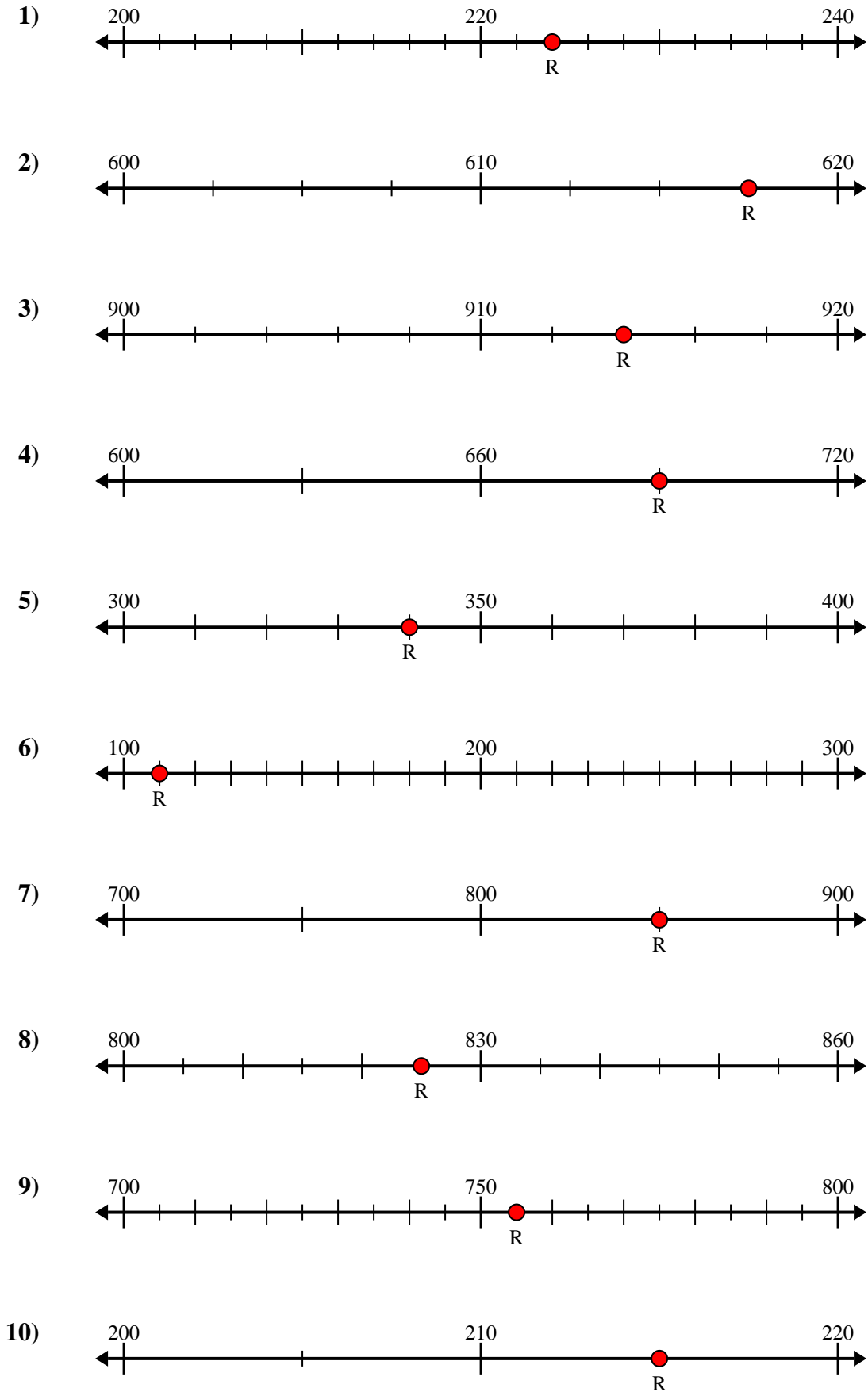

Answers

1. 224
2. 618
3. 914
4. 690
5. 340
6. 110
7. 850
8. 825
9. 755
10. 215