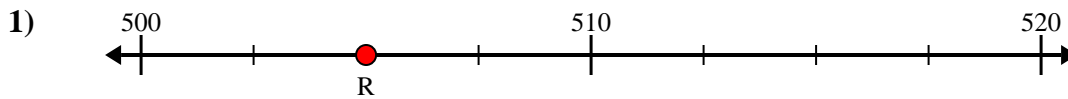





Find the value of R.


Answers




1. \_\_\_\_\_

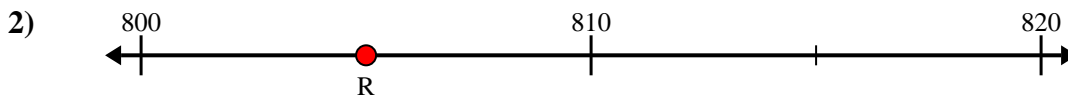


2. \_\_\_\_\_

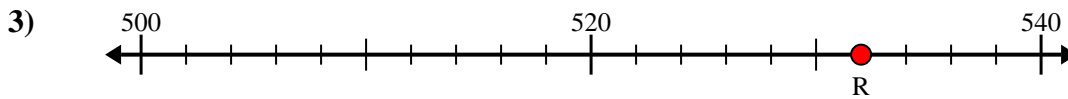


3. \_\_\_\_\_

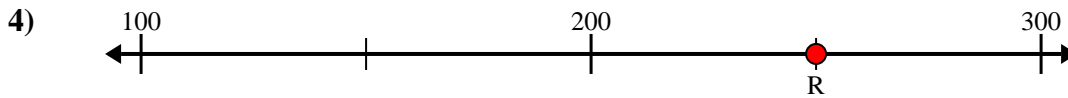


4. \_\_\_\_\_

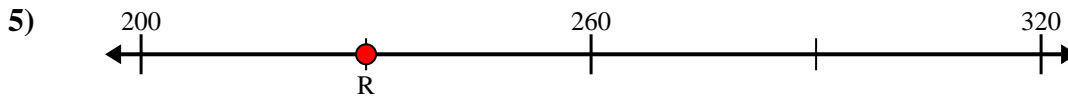


5. \_\_\_\_\_

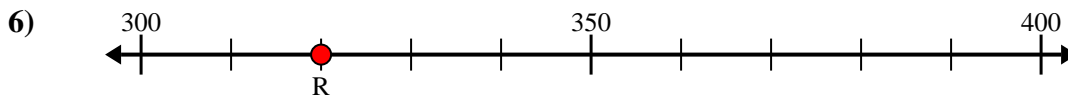


6. \_\_\_\_\_

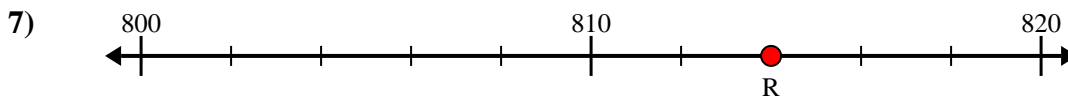


7. \_\_\_\_\_

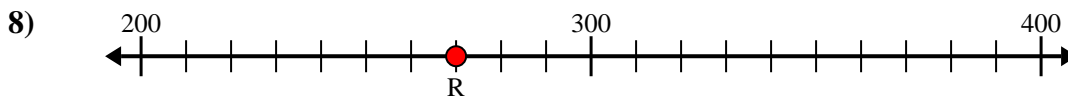

8. \_\_\_\_\_

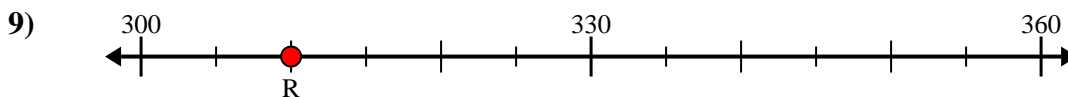











9. \_\_\_\_\_

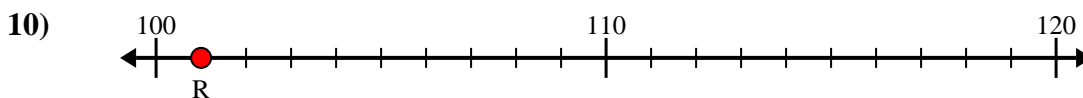

10. \_\_\_\_\_



Find the value of R.

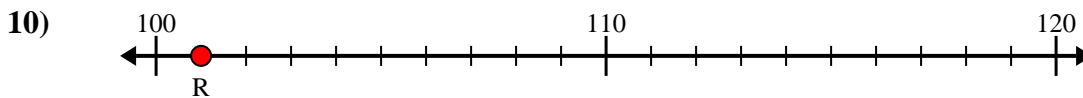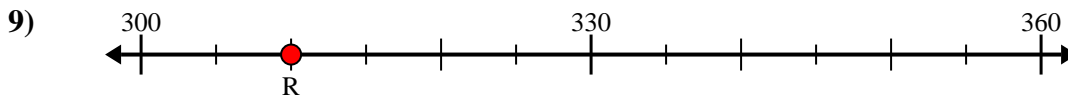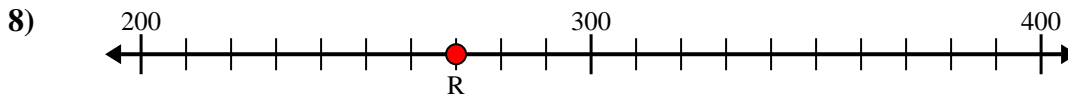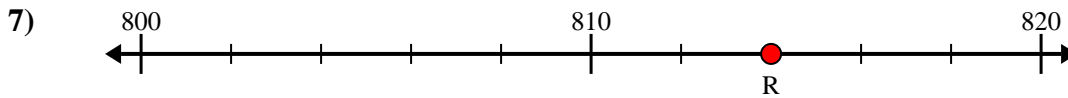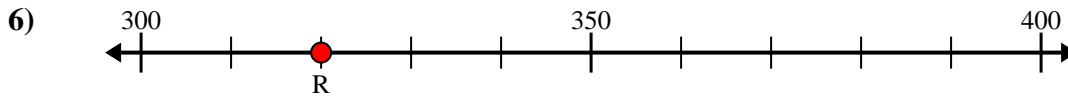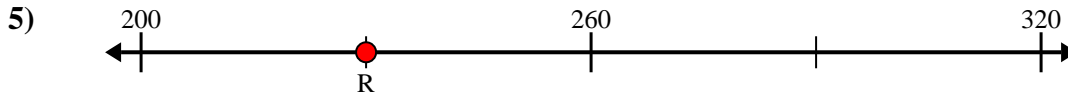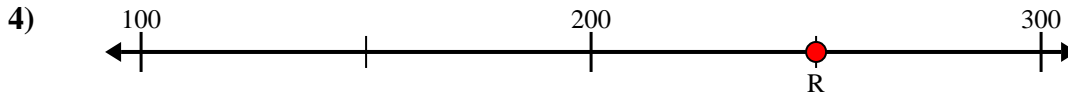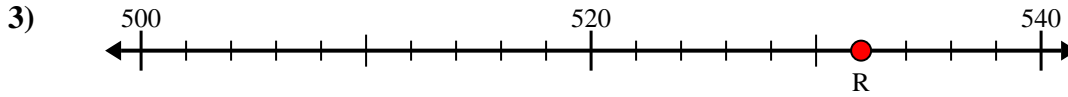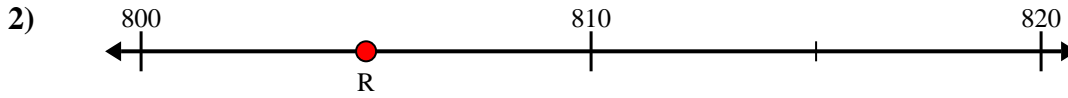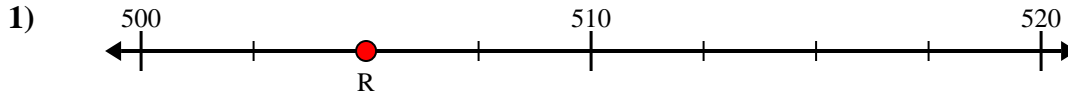

Answers

1. 505

2. 805

3. 532

4. 250

5. 230

6. 320

7. 814

8. 270

9. 310

10. 101