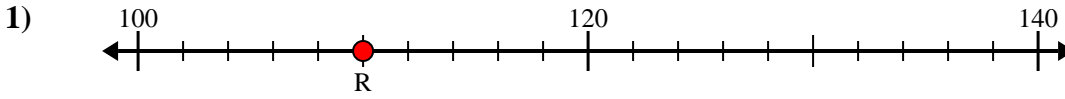





Find the value of R.


Answers




1. _____

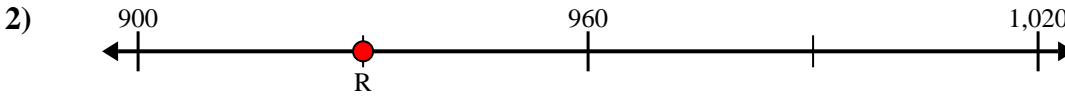


2. _____

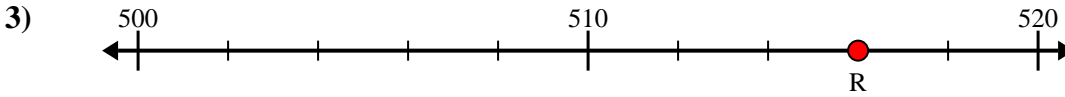


3. _____

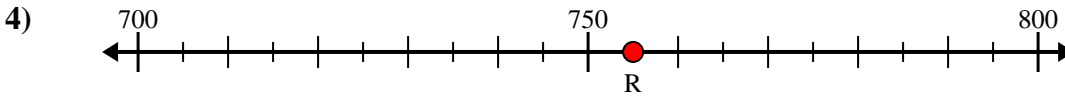


4. _____

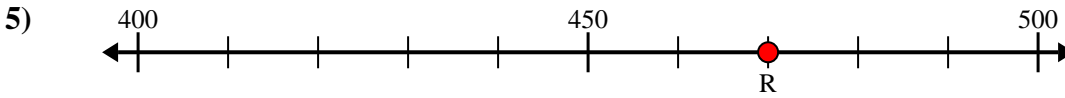


5. _____

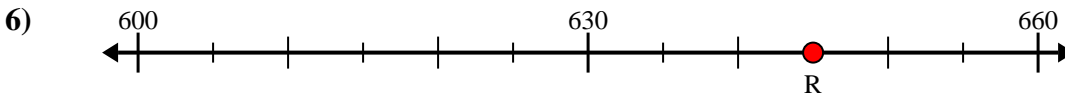


6. _____

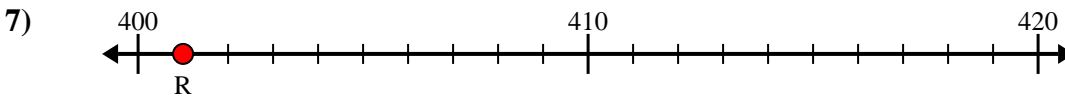


7. _____

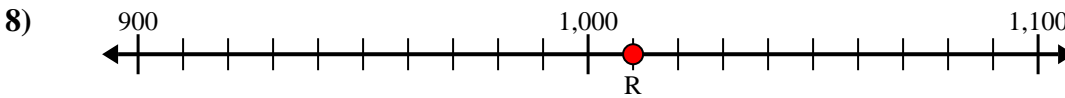

8. _____

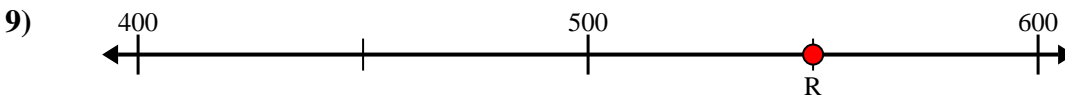


9. _____

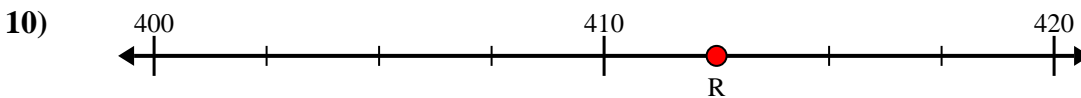

10. _____



Find the value of R.

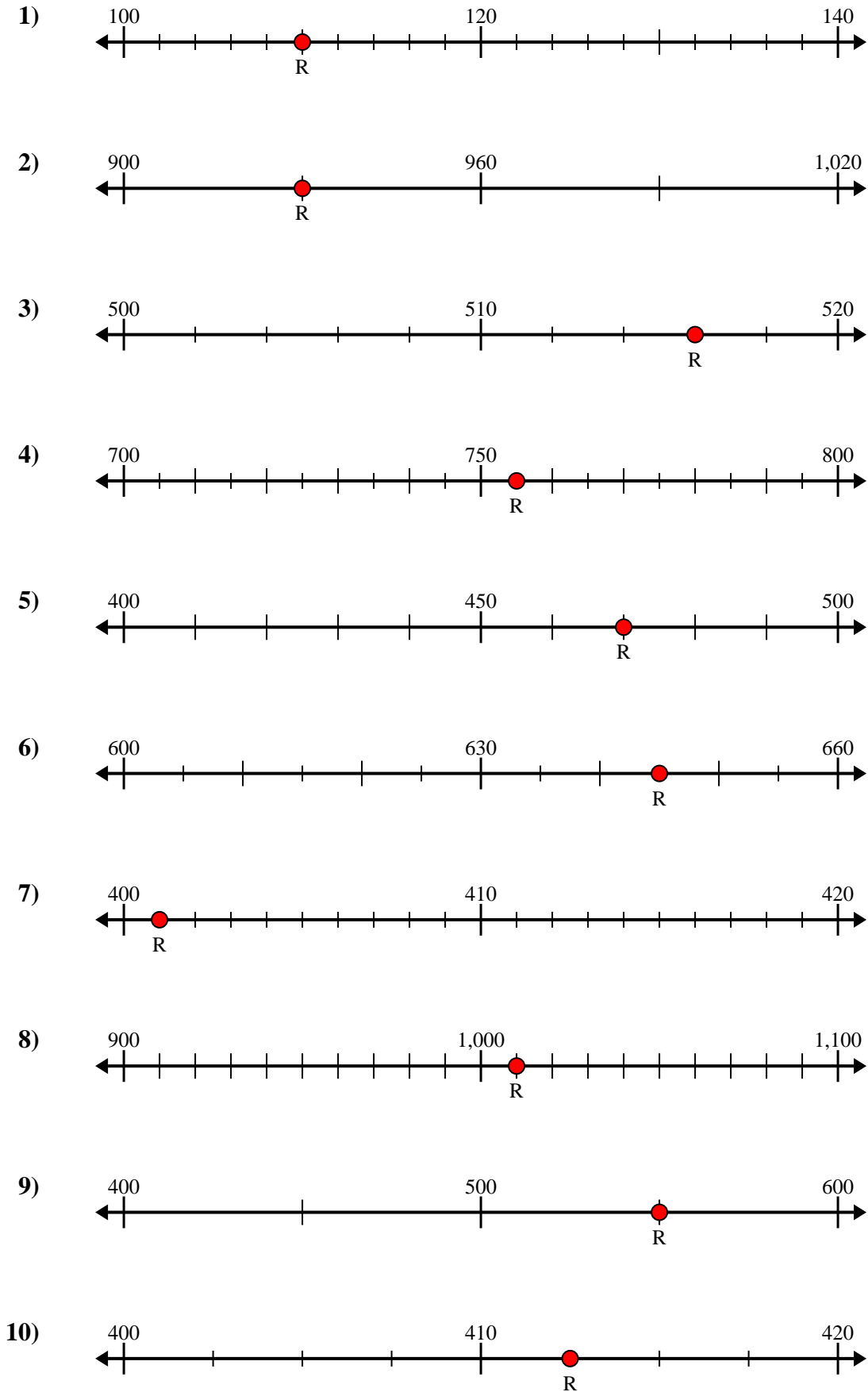

Answers

1. 110
2. 930
3. 516
4. 755
5. 470
6. 645
7. 401
8. 1,010
9. 550
10. 413